

PHY2054 Summer 2018
Lecture 7 Review Questions

Douglas H. Laurence

Department of Physical Sciences, Broward College, Davie, FL 33314

Chapter 21: Electric Current and Direct Current Circuits

Review the following problems (challenge problems given by *):

- **Section 21.1:** 1
- **Section 21.2:** 7*, 9, 21*
- **Section 21.3:** Look at figures 21-40, 21-41, 21-42, and 21-44, and identify which resistors have series connections and which resistors have parallel connections.